
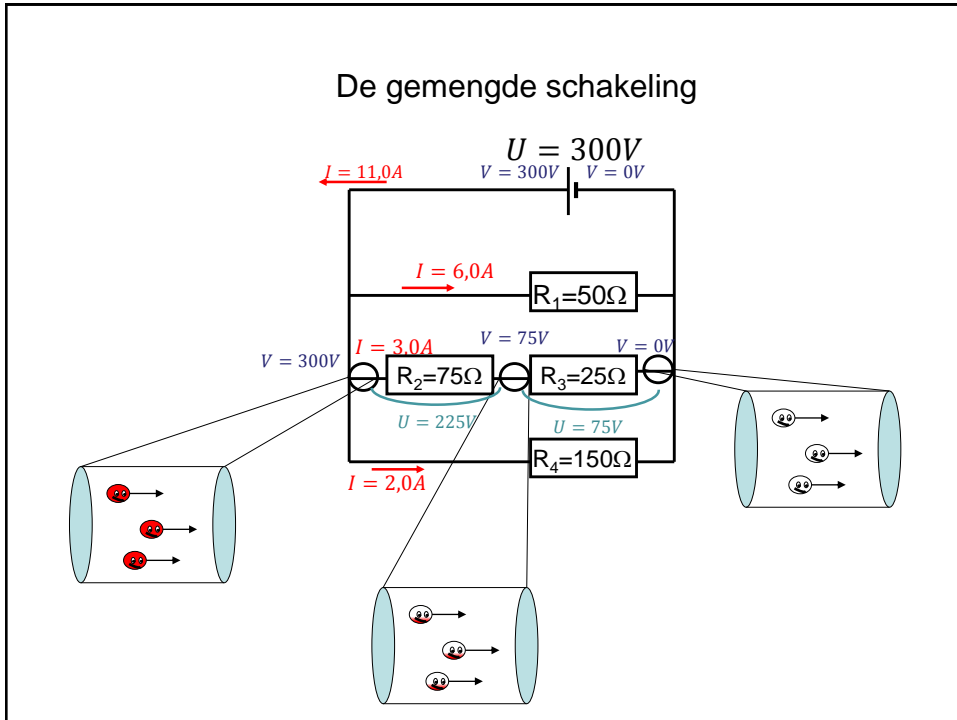


De gemengde schakeling

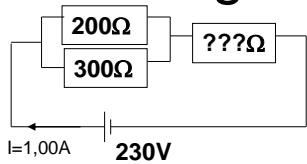

De gemengde schakeling



	R_s	R_1	R_2	R_3
$U(V)$	230	120	120	110
$I(A)$	1,00	0,600	0,400	1,00
$R(\Omega)$	230	200	300	110

$$R_s = \frac{230}{1,00} = 230\Omega \quad \frac{1}{R_{s_{1,2}}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{200} + \frac{1}{300} = \frac{5}{600} \Rightarrow R_{s_{1,2}} = 120\Omega$$

$$R_s = R_{s_{1,2}} + R_3 \quad 230\Omega = 120\Omega + R_3 \quad R_3 = 110\Omega$$

$$I_s = 1,00A \Rightarrow I_3 = 1,00A$$

$$U_3 = I_3 \cdot R_3 = 1,00A \cdot 110\Omega = 110V \quad U_s = U_{1/2} + U_3 \Rightarrow U_{1/2} = 120V$$

$$I_1 = \frac{120}{200} = 0,600A$$

$$I_2 = \frac{120}{300} = 0,400A$$